

# ECE 2700

## Digital Circuits

### Logic Simplifications




Copyright © 2010 Frank Vahid

*Instructors of courses requiring Vahid's Digital Design textbook (published by John Wiley and Sons) have permission to modify and use these slides for customary course-related activities, subject to keeping this copyright notice in place and unmodified. These slides may be posted as unanimated pdf versions on publicly-accessible course websites.. PowerPoint source (or pdf with animations) may not be posted to publicly-accessible websites, but may be posted for students on internal protected sites or distributed directly to students by other electronic means. Instructors may make printouts of the slides available to students for a reasonable photocopying charge, without incurring royalties. Any other use requires explicit permission. Instructors may obtain PowerPoint source or obtain special use permissions from Wiley – see <http://www.drvahid.com> for information.*

# Today's Objectives

- To deepen your understanding on how to use Boolean Algebra to simplify/convert/manipulate digital circuits
- To understand the difference between optimization and tradeoff

# Representations of Boolean Functions

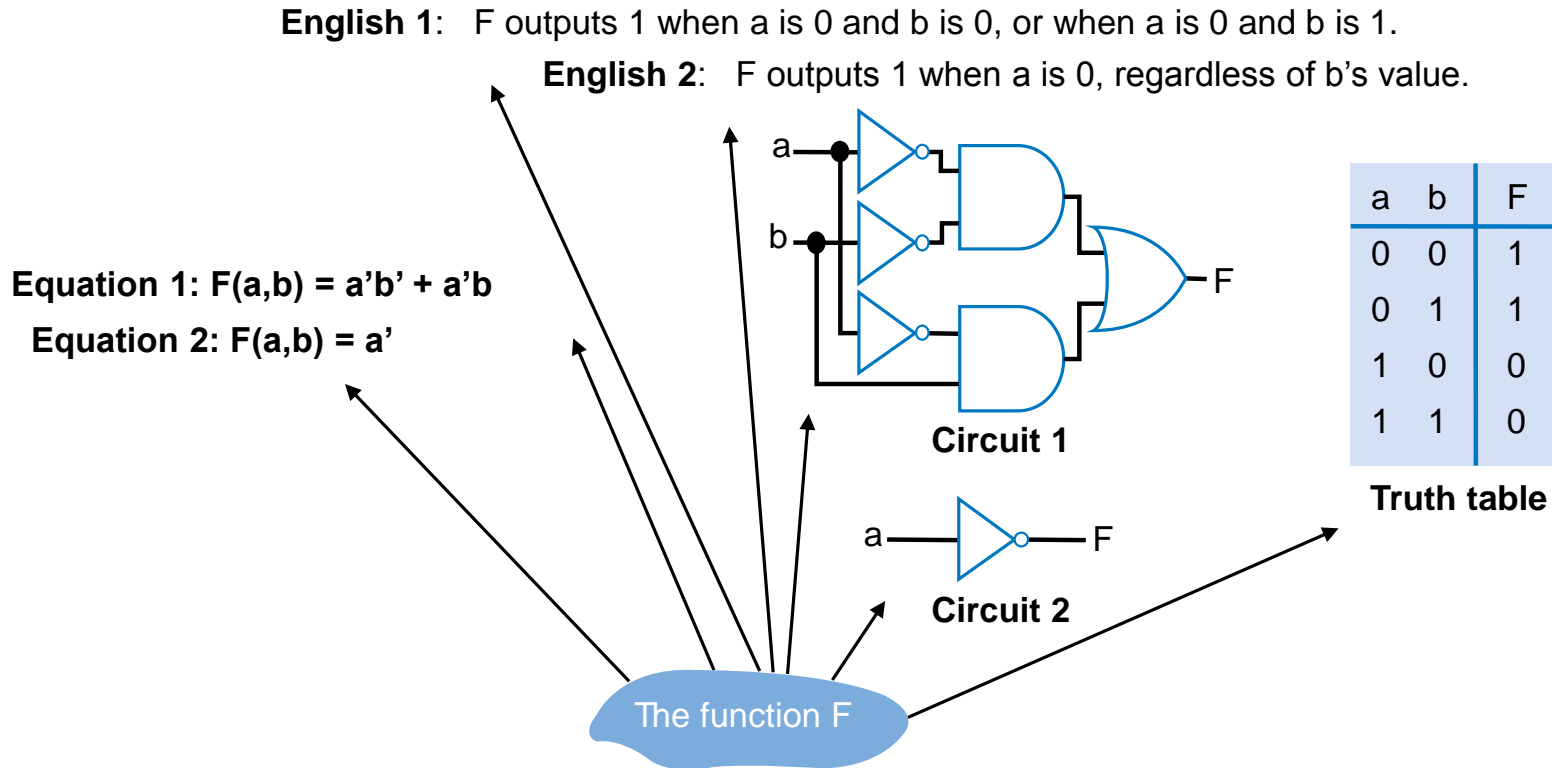

- Only one truth table for any given Boolean function

# Truth Table Representations

a	b	F
0	0	
0	1	
1	0	
1	1	

a	b	c	F
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

a	b	c	d	F
0	0	0	0	
0	0	0	1	
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

- Can be tedious as number of variables exceeds 5

# Question (AP)


- Using truth tables, are F and G equivalent?
  - $F = xy + xy' + y'z$
  - $G = yz + x'z'$

A. Yes

B. No


C. ☹️

# Converting among Representations

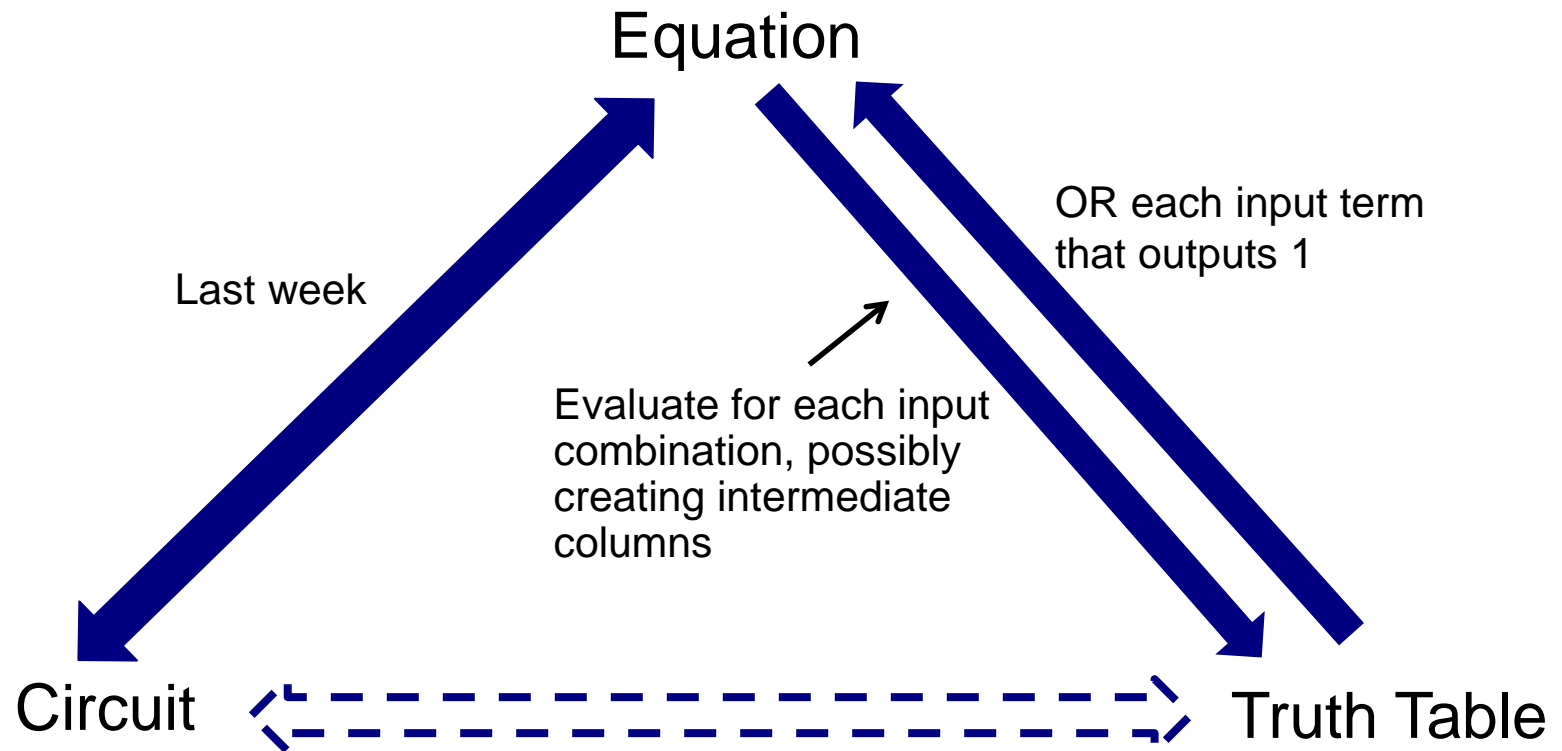
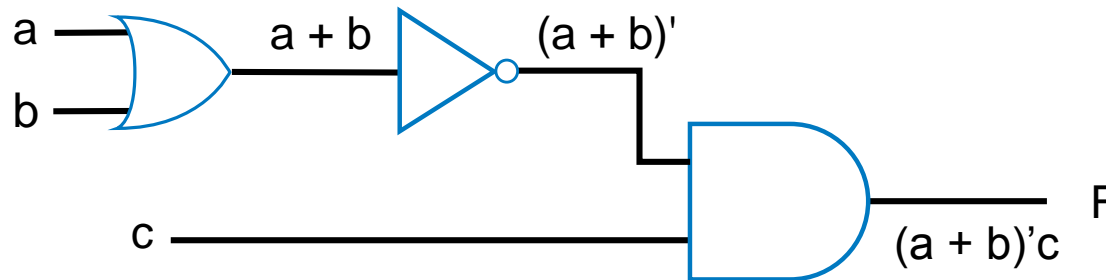
# Circuit to Truth Table



- First convert to circuit to equation, then equation to table



Inputs					Outputs
a	b	c	$a + b$	$(a + b)'$	F
0	0	0	0	1	0
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	0	0
1	1	0	1	0	0
1	1	1	1	0	0

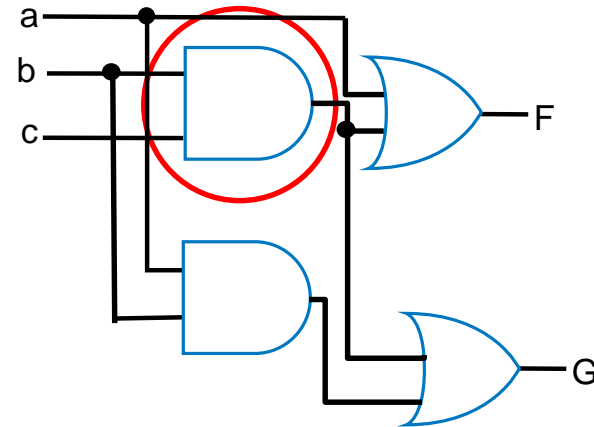
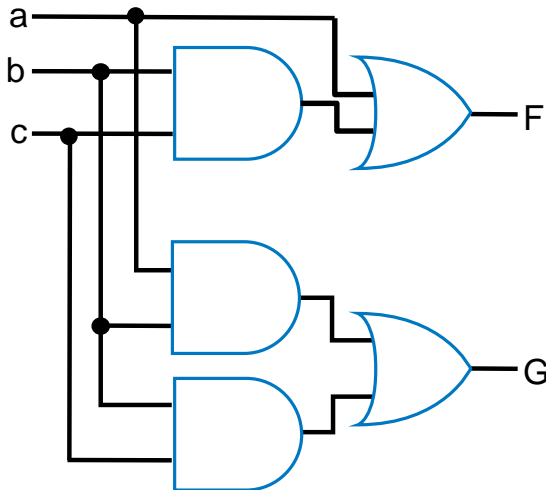
# Multiple-Output Circuits

- Can give each a separate circuit, or can share gates
- Example:  $F = a + bc$ ,  $G = ab + bc$





# Multiple-Output Example

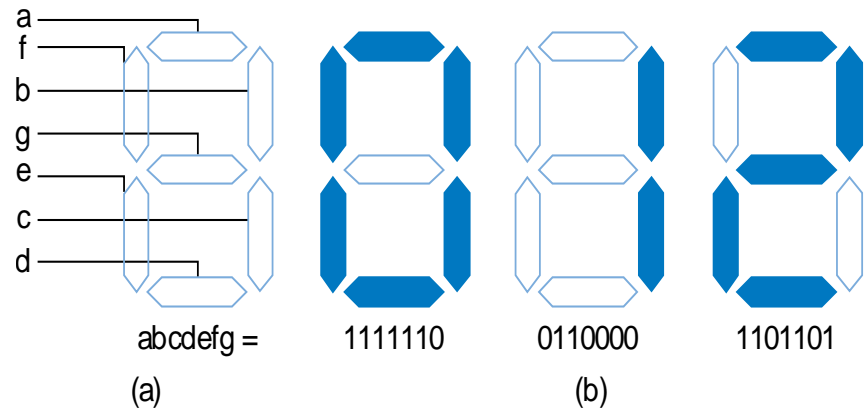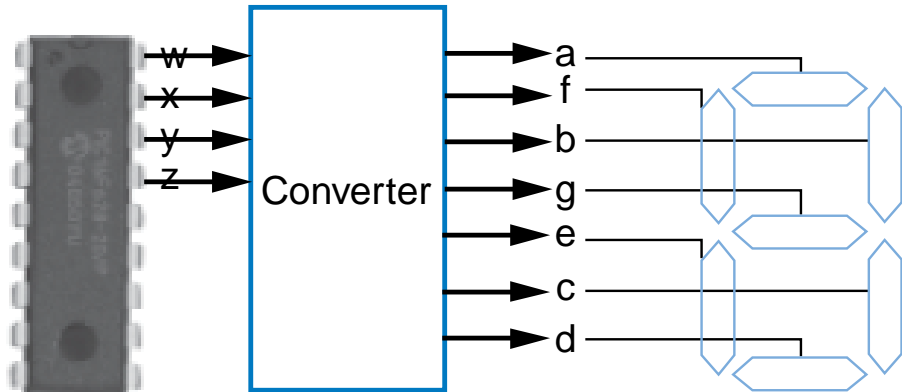

# Boolean Equations in Canonical Form

- (Standard form)
- Regular algebra: how do you know if the following equations are equivalent?
  - $F = 5x^2 + 4x + 4$
  - $G = 3x^2 + 4x + 2x^2 + 3 + 1$
- Boolean algebra: create sum of minterms
  - Minterm: product term with every literal appearing exactly once, in true or complemented form

# Minterms for Three Variables

x	y	z	Mystery Function	Minterm
0	0	0		$x'y'z'$
0	0	1		$x'y'z$
0	1	0		$x'yz'$
0	1	1		$x'yz$
1	0	0		$xy'z'$
1	0	1		$xy'z$
1	1	0		$xyz'$
1	1	1		$xyz$

- $F = x'y'z' + x'y'z + xy'z' + xyz'$ 
  - F is in canonical form (sum of minterms)

# Writing a Boolean Eqn. in Canonical Form

- Steps
  - Obtain sum of product terms by multiplying-out equation
  - Expand each term until all terms are minterms
- Can be handy when you need to compare two equations


# Building Better Circuits

- Two important design criteria
  - Delay – the time from inputs changing to new correct stable output
  - Size – the number of transistors
  - Ideally, we want a small circuit with a small delay
- For quick estimation, assume
  - Every gate has delay of “1 gate-delay”
  - Every gate input requires 2 transistors
    - Ignore inverters

# Optimization


- $F = (x + y)z + y'z$

- $G = z$

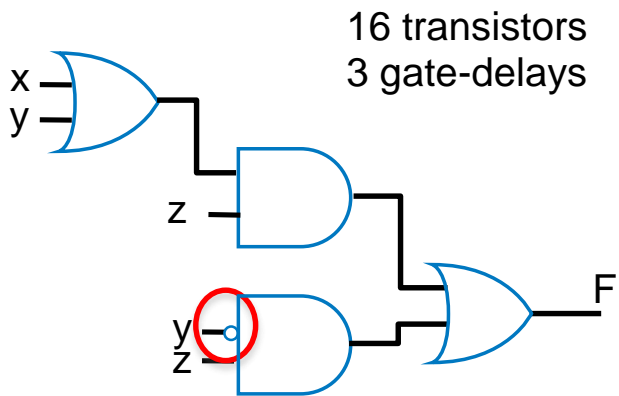

$z \text{ --- } G$

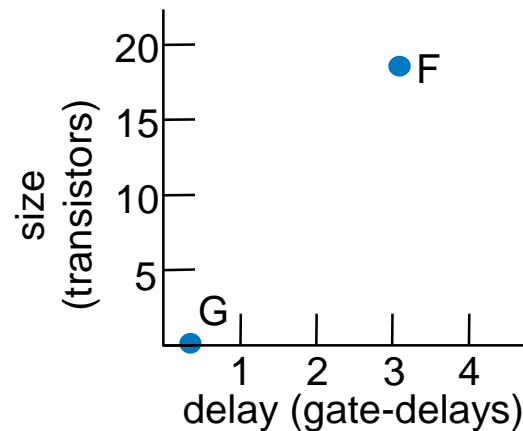
0 transistors  
No gate-delay (only wire delay)





Transforming F to G represents an **optimization**: Better in all criteria of interest

# Tradeoff

- $F = a + bc + cd$

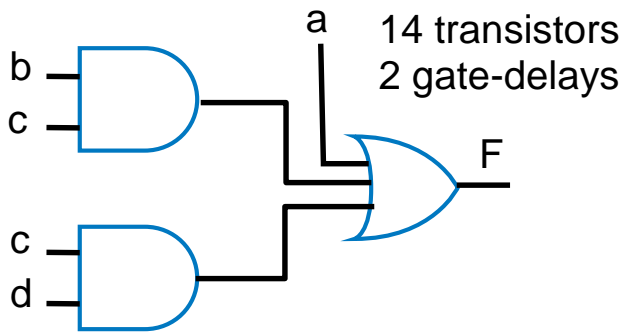

- $G = a + c(b + d)$

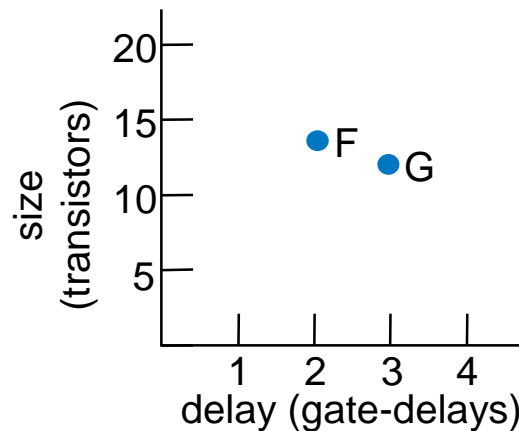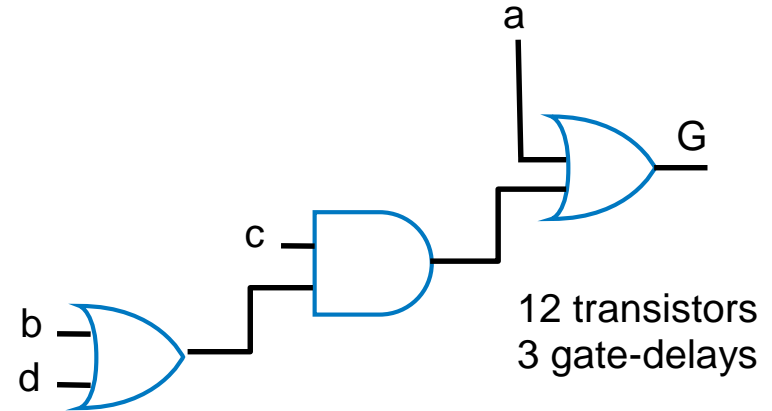

Transforming  $F$  to  $G$  represents an **tradeoff**. Some criteria better, others worse

# Question (AP)

- How many transistors does the following circuit have?
  - $F = xy + x'y' + w$
  - 10
  - 12
  - 14
  - 16
  - ☹️



# Question (AP)

- What is the number of gate delays for the following circuit assuming each gate has 2 inputs?

–  $F = xy + x'y' + w$

A.0

B.1

C.2


D.3

E.4

# Optimization vs. Tradeoff

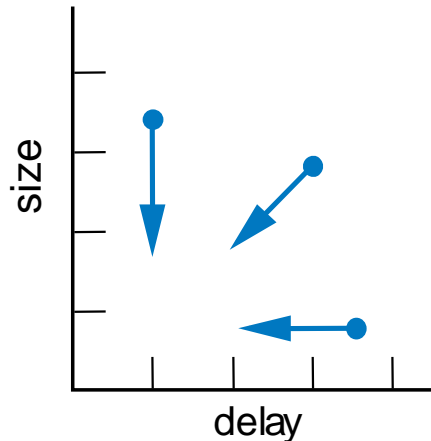
## **Optimizations**

All criteria of interest are improved (or at least kept the same)


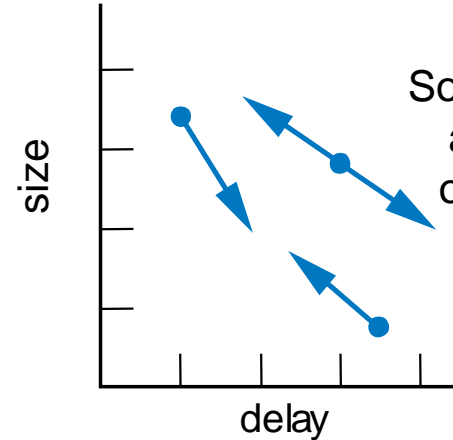
## **Tradeoffs**



Some criteria of interest are improved, while others are worsened



- We obviously prefer optimizations, but often must accept tradeoffs
  - You can't build a car that is the most comfortable, and has the best fuel efficiency, and is the fastest – you have to give up something to gain other things
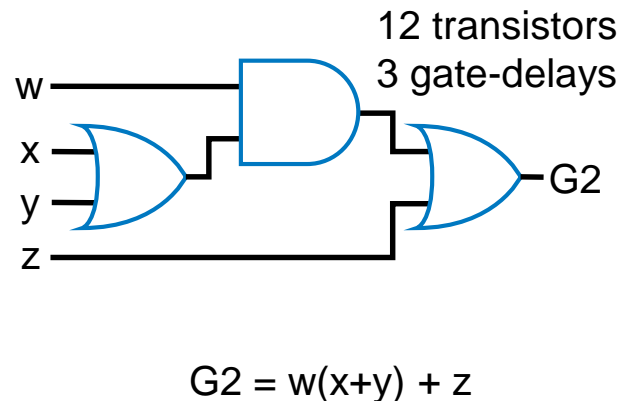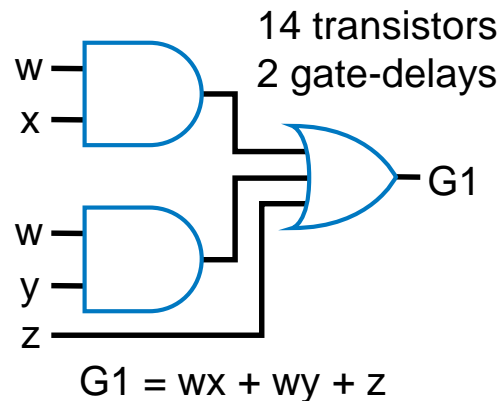
# How To Determine Which Options Is Better?


- Usually specified by your client, boss, etc...




# Other Design Criteria

- Power
- Temperature
- Many others...

# Temperature Concern

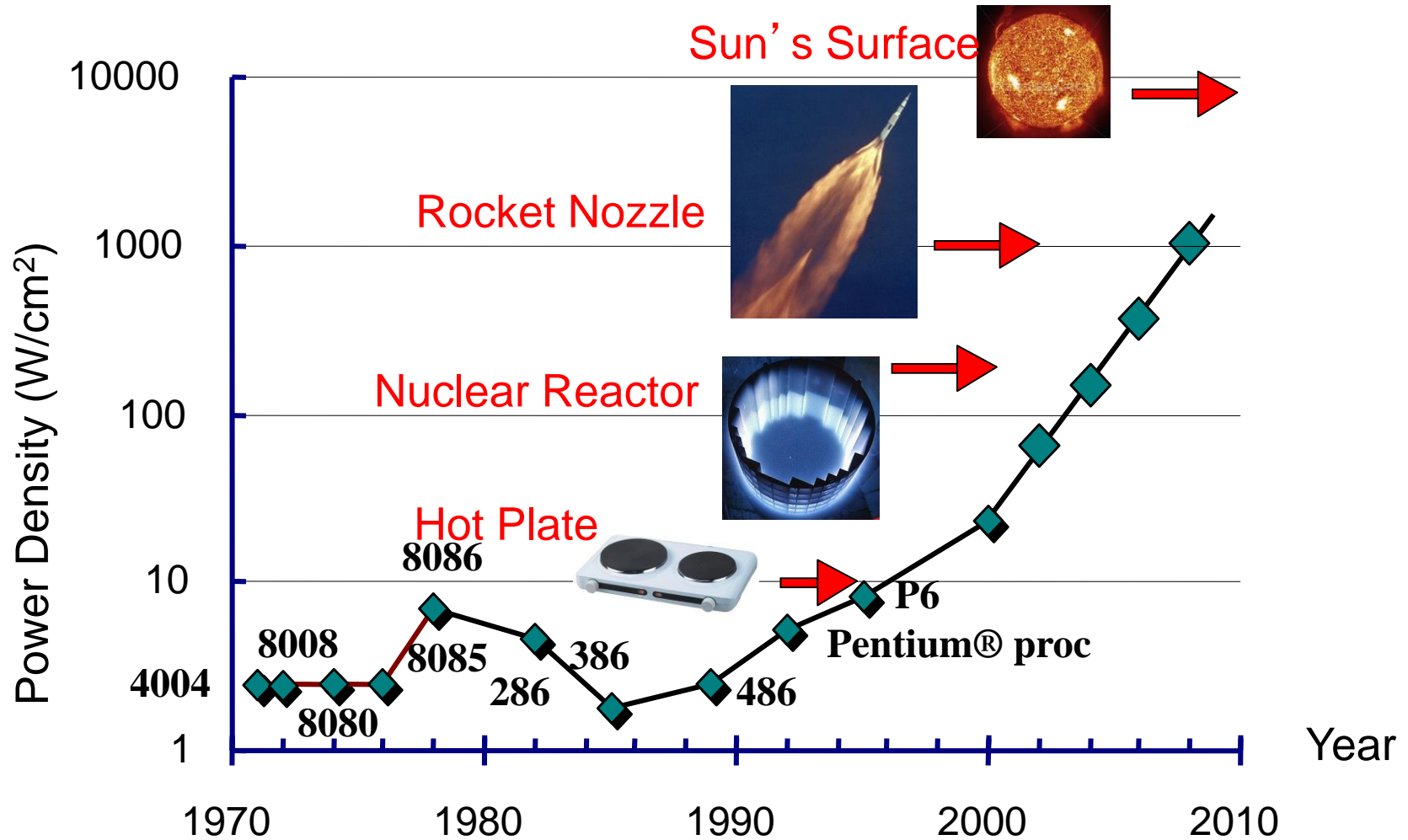

# Battery Capacity

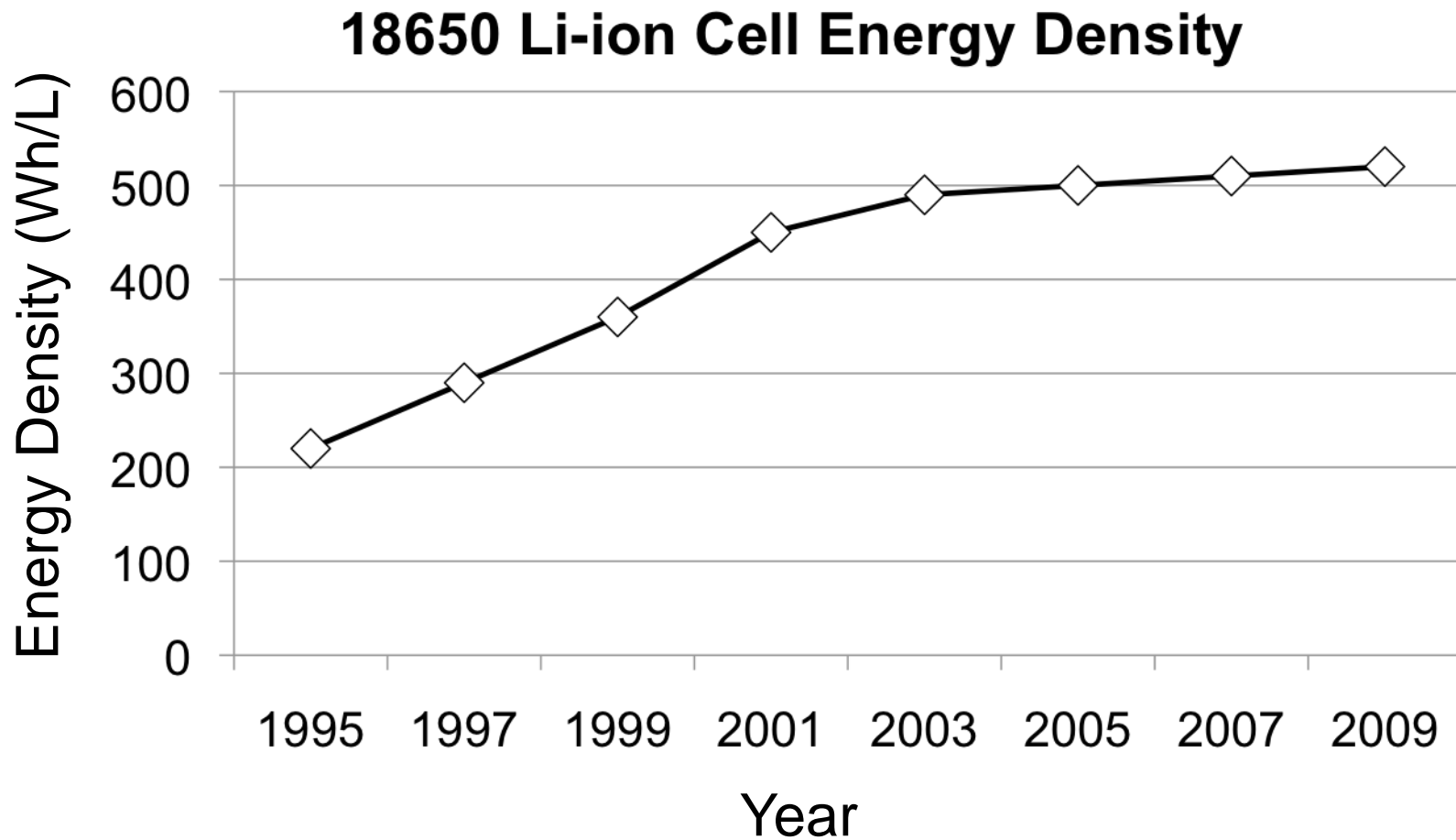

# Our Focus

- Two-level size optimization using algebraic methods
  - Two-level circuit (ORed AND gates) with fewest transistors
  - Though transistors getting cheaper (Moore's Law), still cost something
- Remember **sum-of-products**?
  - $F = abc + abc'$  is sum-of-products
  - $G = w(xy + z)$  is not
- Transform sum-of-products equation to have fewest literals and terms

# Algebraic Two-Level Size Optimization (1)

- Multiply out to sum-of-products, then...
- Apply following as much as possible
  - $ab + ab' = a(b + b') = a \cdot 1 = a$ 
    - Combining terms to eliminate a variable
    - (Formally called the “Uniting theorem”)
- Sometimes after combining terms, can combine resulting terms

$$F = ab'c' + ab'c + abc' + abc$$

$$F = ab'(c' + c) + ab(c' + c)$$

$$F = ab' \cdot 1 + ab \cdot 1$$

$$F = ab' + ab$$

$$F = a(b' + b)$$

$$F = a \cdot 1$$

$$F = a$$



# Algebraic Two-Level Size Optimization (2)

- Duplicating a term sometimes helps
  - Doesn't change function
  - $c + d = c + d + d = c + d + d + d + d \dots$

$$F = ab'c' + ab'c + abc' + abc + a'bc$$

$$F = ab'c' + ab'c + abc' + abc + a'bc + \mathbf{abc}$$

$$F = ab'(c' + c) + ab(c' + c) + (a' + a)bc$$

$$F = ab'*\mathbf{1} + ab*\mathbf{1} + \mathbf{1}*bc$$

$$F = ab' + ab + bc$$

$$F = a(b' + b) + bc$$

$$F = a*\mathbf{1} + bc$$

$$F = a + bc$$

# Algebraic Two-Level Size Optimization (3)

- Sometimes, it may be hard to see opportunities to simplify equations
  - There are no hard and fast rules on how to simplify an expression
  - Can we guarantee success?
- Use a pictorial form of truth table!

# Today's Objectives

- To deepen your understanding on how to use Boolean Algebra to simplify/convert/manipulate digital circuits
- To understand the difference between optimization and tradeoff

# Question

- What's the canonical form of the following Boolean equation?

$$F = abc + bc$$